


EEO 401
Digital Signal Processing
Prof. Mark Fowler

Note Set #17

- Oversampling ADCs
- Reading Assignment: Sect. 6.6 of Proakis & Manolakis

Trading BW for Bits


- **Oversample and Filter:**
 - Say You Have an ADC That Can Sample at a Rate of F_s .
 - Quantization Noise PSD is Uniformly Spread Over $-F_s/2$ to $F_s/2$.
 - If Signal Resides in Some Subband, Digitally Filter to that Band:
 - Signal Power Same, but Noise Power Reduced → **Improves the SNR**
 - But... SNR is related to ENOB → **Increases the Effective # of Bits!**
 - Analogous to averaging a bunch of integers to get a fractional value
 - **Increased ENOB** at the Expense of **Reduced Processing BW**

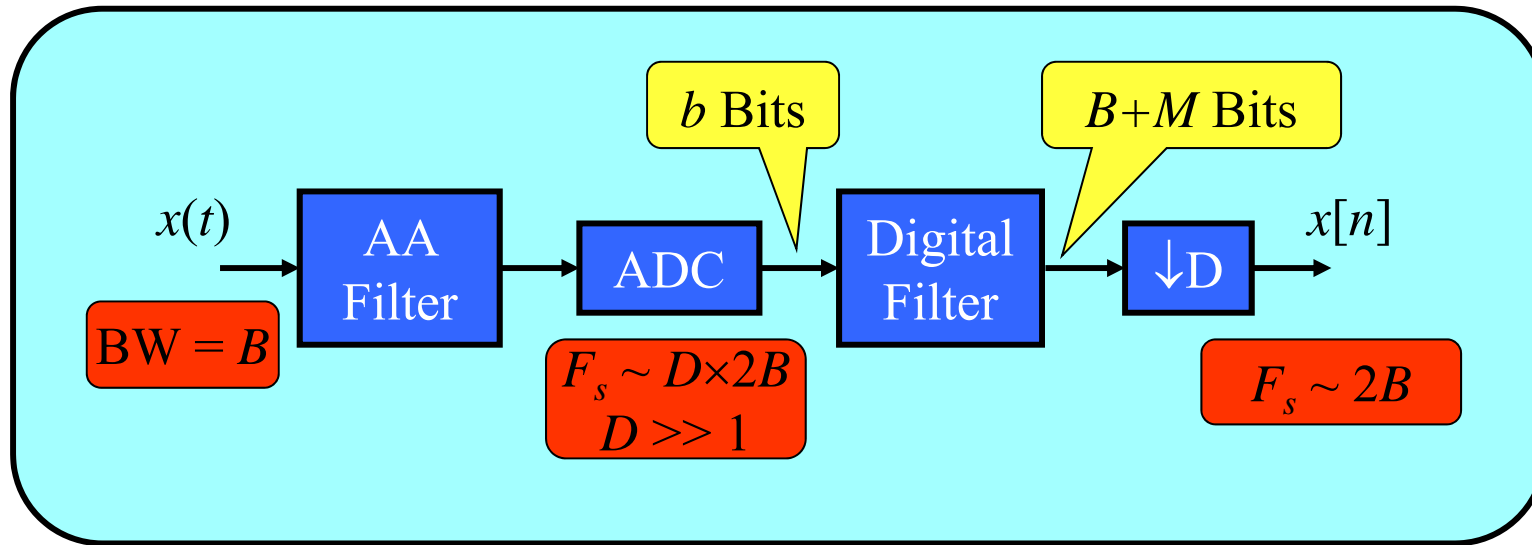

Trading BW for Bits

- **Noise Reduction View:**

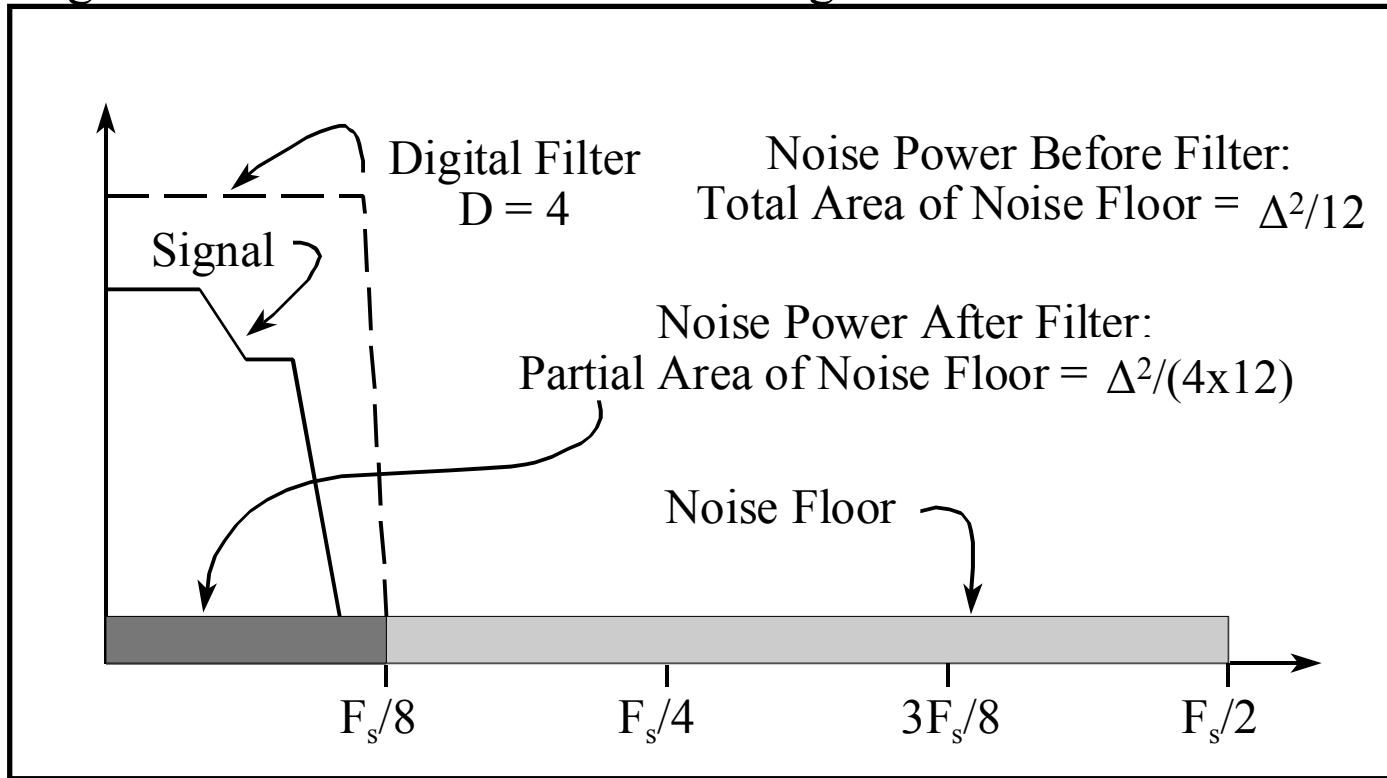- Quantization Noise PSD is Uniformly Spread Over $-F_s/2$ to $F_s/2$.
- Signal is Concentrated in Narrow Region




Quartering BW \rightarrow 6 dB Less Noise \rightarrow 6 dB More SNR \rightarrow 1 More Bit

Trade Rate = $\frac{1}{2}$ Bit per Octave \rightarrow Inefficient Trade!!!

Better Trade: Sigma-Delta ADCs

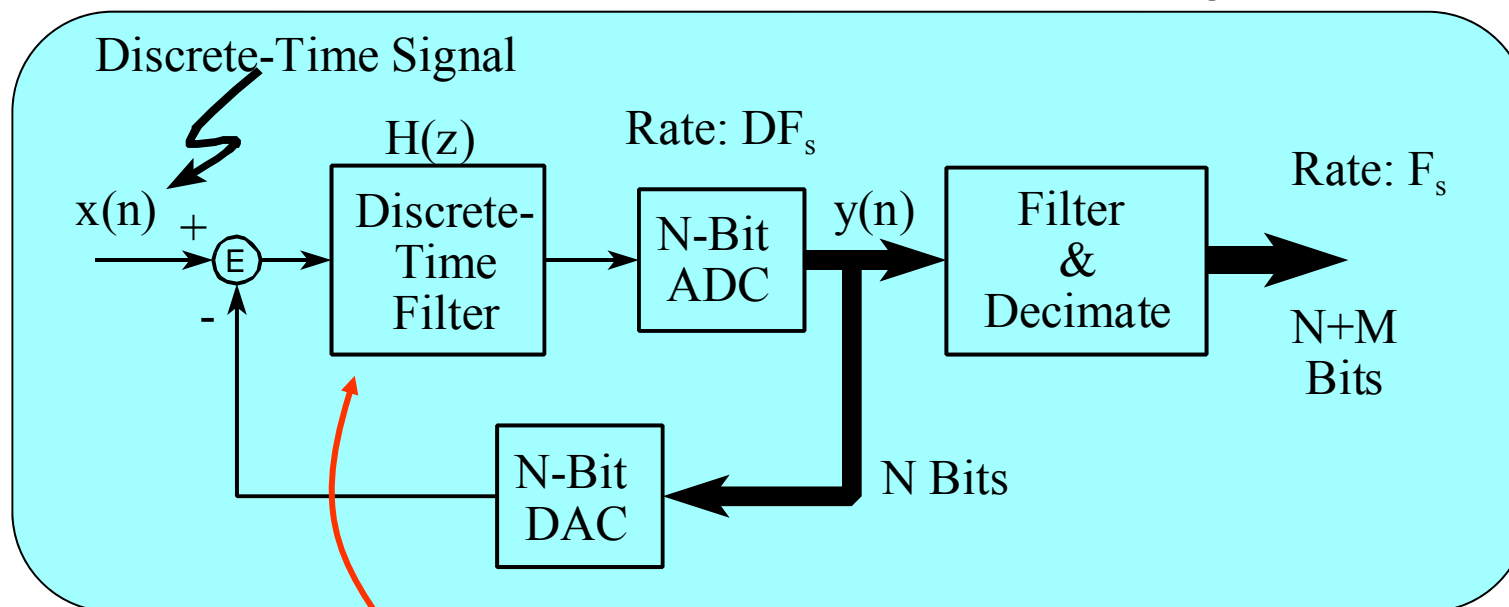
- Use VERY High Over-Sampling Rate
- Use Low-Bit ADC (sometimes even just 1 Bit)
- Use DSP Noise Shaping to Non-Uniformly Spread Noise
 - Push Most of the Quantization Noise Out of the Signal Band




Design Filter $H(z)$ to:

- ▶ Pass Signal w/ Minimal Distortion
- ▶ Attenuate Quantization Noise in Signal Band


Σ - Δ ADC Advantage

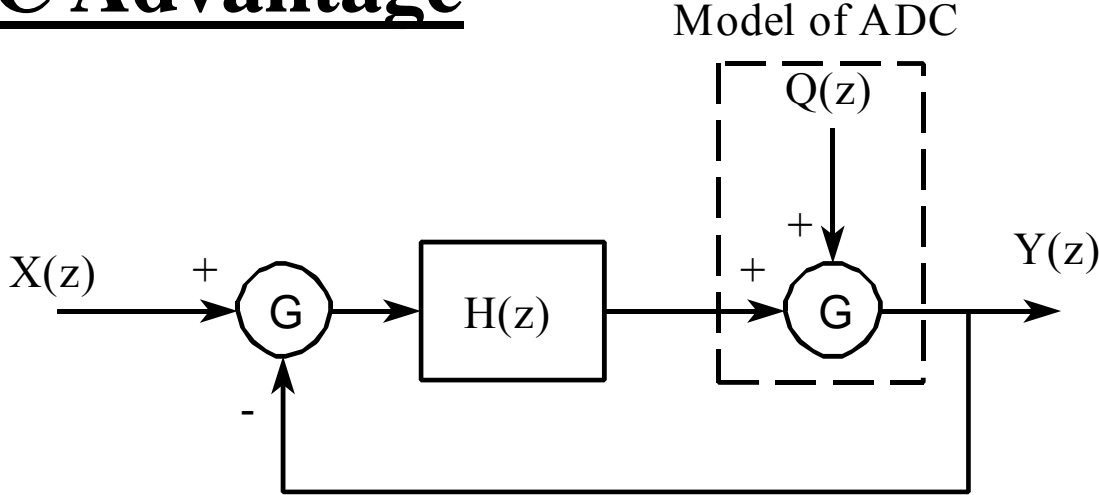
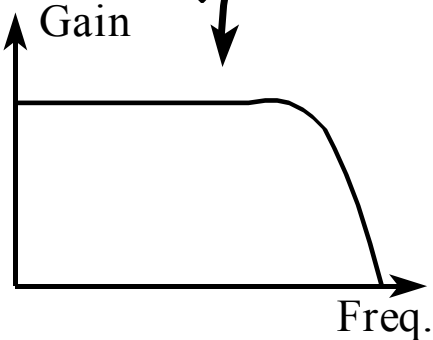
$$Y(z) = \underbrace{\frac{H(z)}{1+H(z)}}_{\text{Signal Transfer Function}} X(z) + \underbrace{\frac{1}{1+H(z)}}_{\text{Noise Transfer Function}} Q(z)$$




Signal Transfer Function

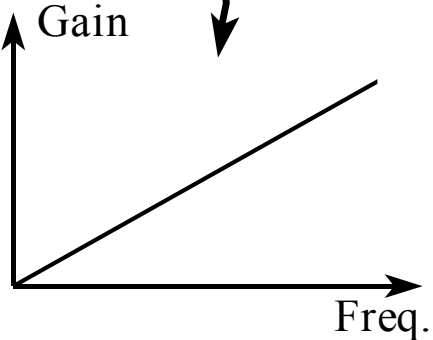

Noise Transfer Function


Σ - Δ ADC Performance

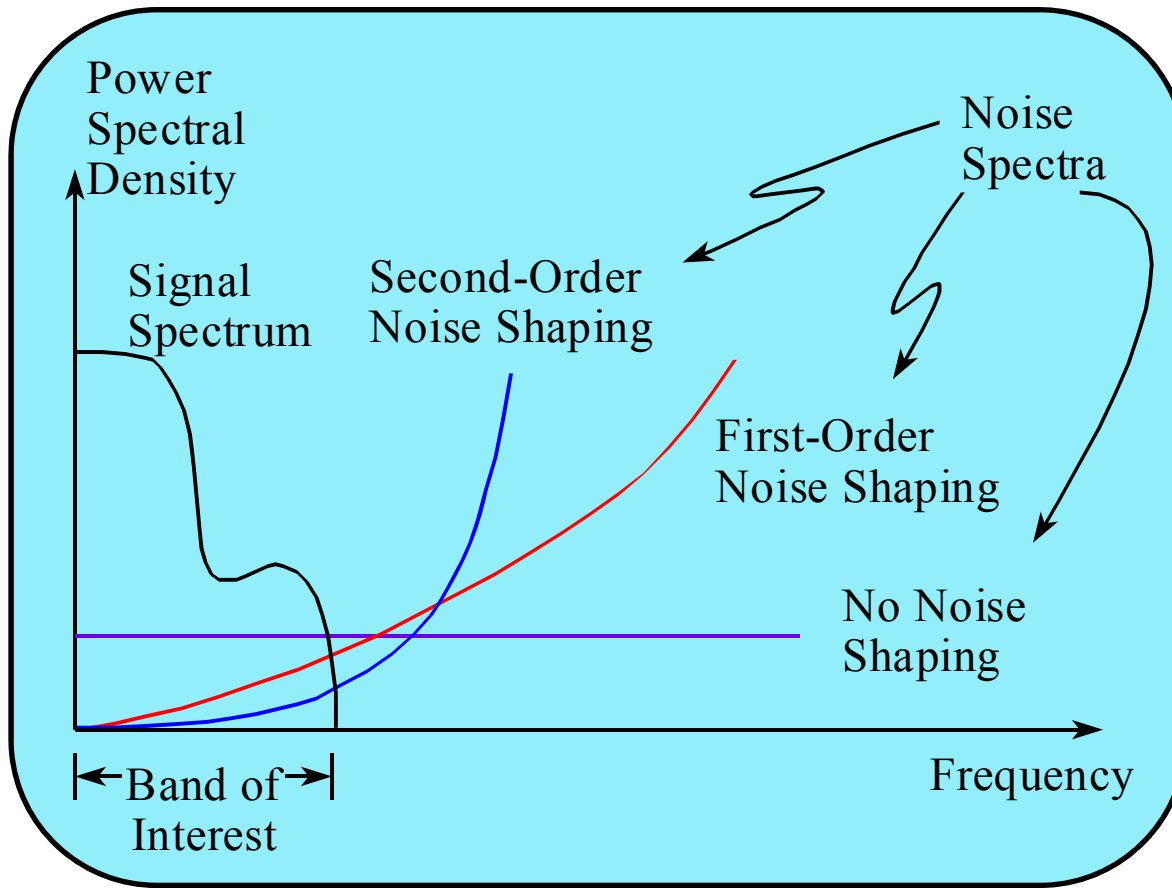- Two Main Factors Impact Performance:
 - Oversampling Rate D
 - Order of the Noise Shaping (1st, 2nd, 3rd, etc.)



Noise Shaping	Trade Rate
None	0.5 Bits/Octave
1 st Order	1.5 Bits/Octave
2 nd Order	2.5 Bits/Octave

Σ - Δ ADC Performance

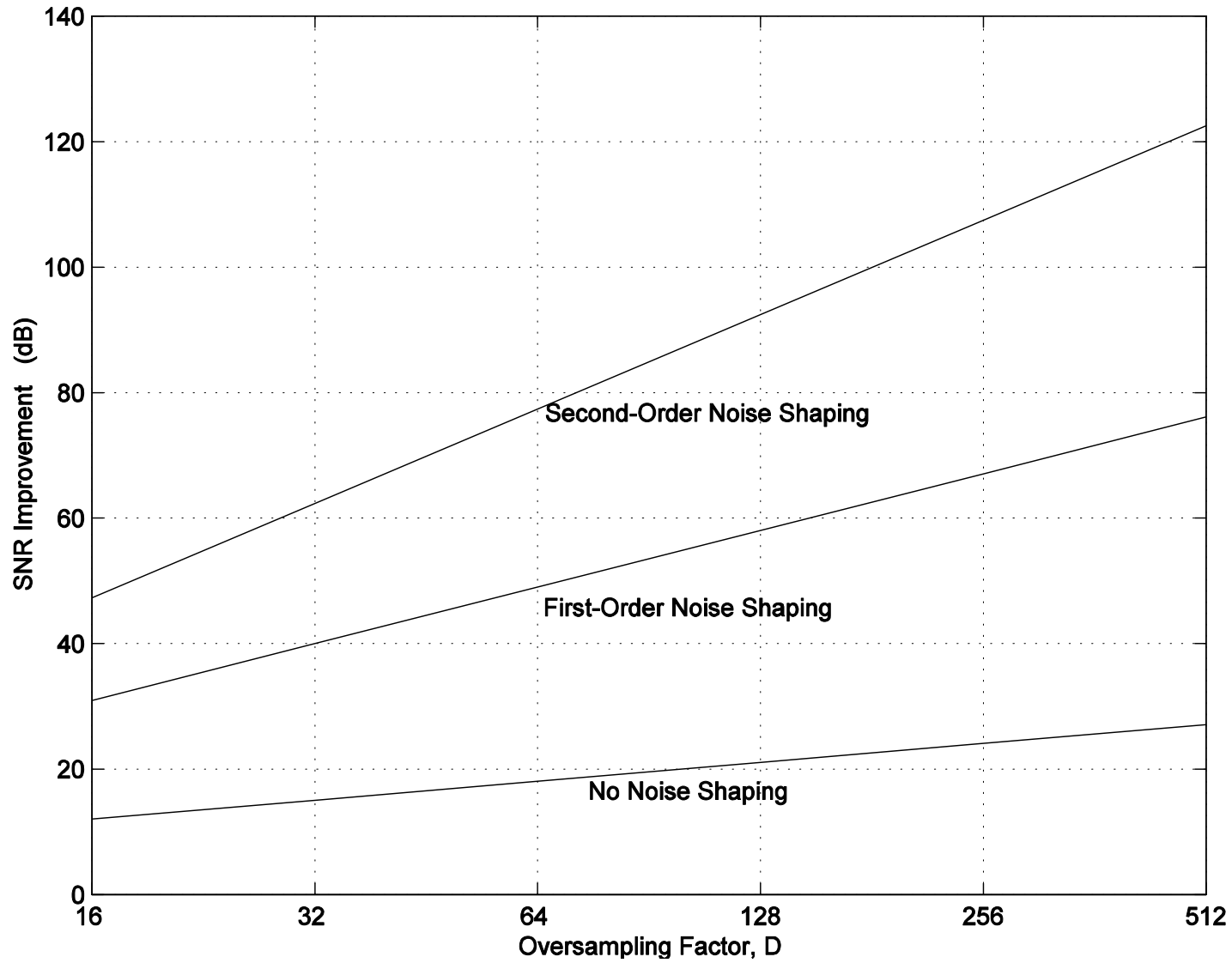

Σ - Δ ADC Summary

- Advantages of Sigma-Delta ADCs is Three-Fold:
 - Oversampling makes the Anti-Alias Filter Easy!
 - Noise Shaping Pushes ADC Noise Outside Signal Band
 - Low-Bit ADCs can be Made Closer to Ideal than High-Bit ADCs
- Disadvantage
 - Hard to get Extremely Wide Processing BW
 - But progress is being made...