

EECE 301
Signals & Systems
Prof. Mark Fowler

Note Set #35

- C-T Systems: CT Filters - Passive

Introductory Comments

“CT Filters” are also called “Analog Filters”

Recall that we already talked about ideal CT filters:

- $|H(\omega)|$ is Constant in Pass band
- $|H(\omega)|$ is zero in Stop band (Transition Band has zero width)
- $\angle H(\omega)$ is linear in Pass band

We also saw that such ideal filters can not really exist because they would need to be non-causal!!

Here we'll take a brief look at some of the kinds of CT filters that can be made...

- Note... all CT filter behavior exploits the fact that capacitors and inductors have an impedance that varies with frequency!

And we'll illustrate how to describe such filters using:


- Transfer Function
- Frequency Response
- Pole-Zero Diagrams

Also... keep in mind that although DT filters only need to be examined over $-\pi$ to π rad/*sample* (their Freq Resp repeats outside of that)... CT filters need to be examined for how they behave over $-\infty$ to ∞ rad/*second*. Thus, we will mostly plot them on a log frequency axis... with dB for the magnitude.

Practical Filter Specification


LPF Spec – Version 1

Specs for HPF, BPF, & BSF are similar...

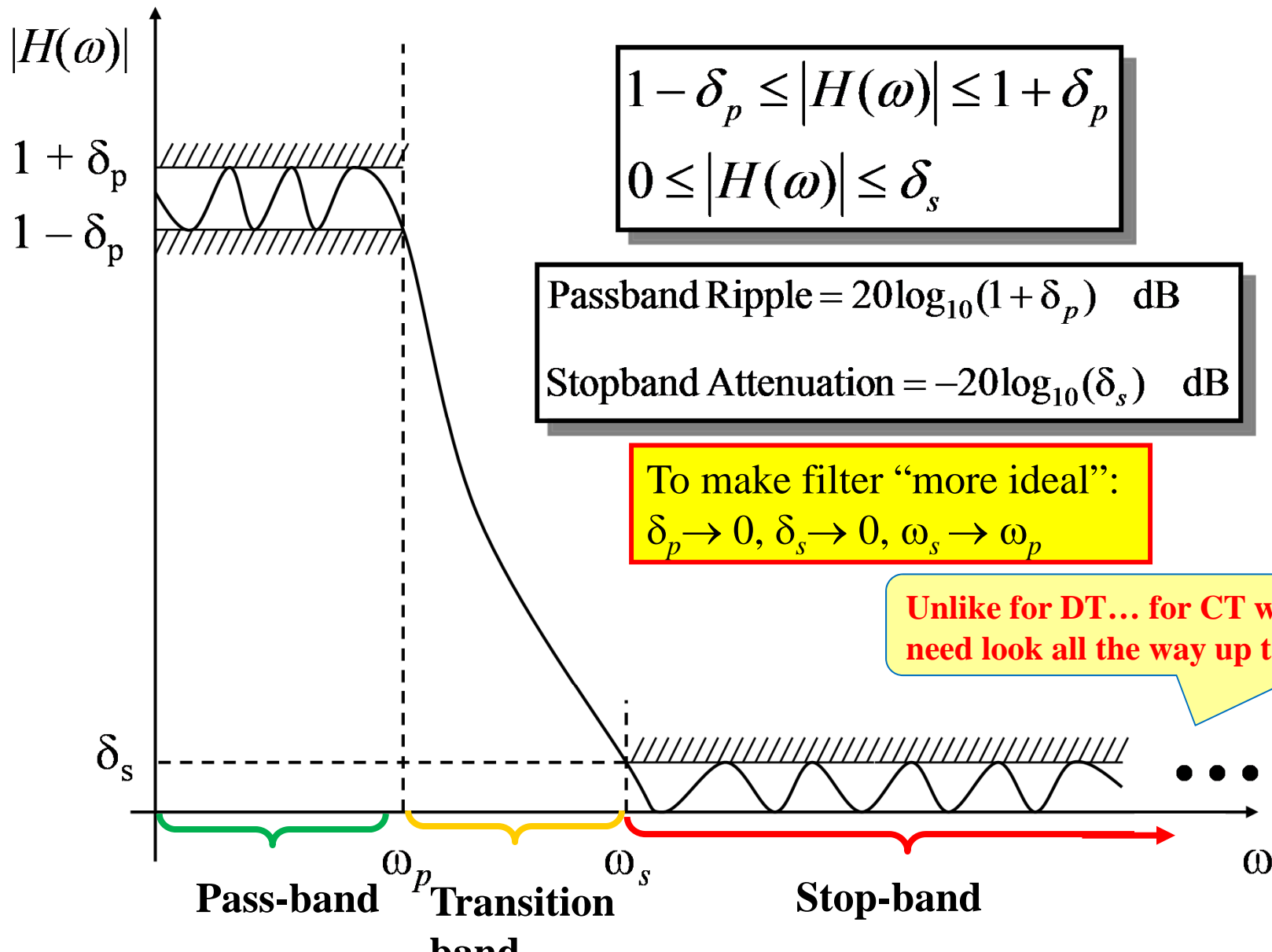

LPF Spec – Version 2

Specs for HPF, BPF, & BSF are similar...

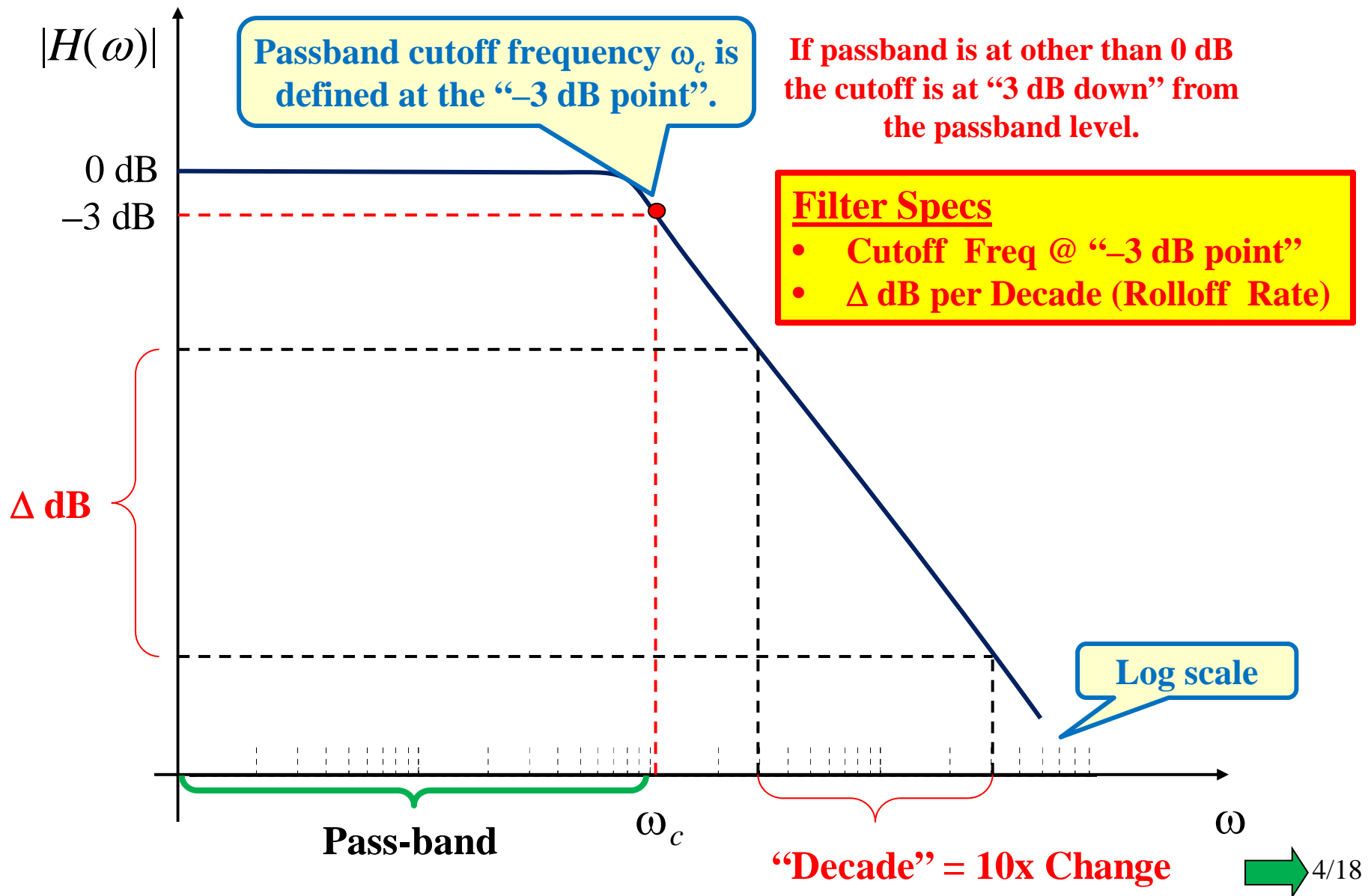

CT Filter Types

Recall that DT filters were categorized as recursive (IIR) vs. non-recursive (FIR).

CT filters don't have a corresponding categorization... they all have infinite duration impulse responses!!!

Instead the main way to categorize CT filters is: Passive vs. Active

Passive: These filters use only “passive components” (resistors, capacitors, and inductors) and do not contain any op amps or transistors.

- One main advantage of such filters is that they can be used in places where access to a power supply is not available (e.g., inside a stereo speaker to separate the audio into bass and treble before sending it to the woofer & tweeter).


Active: These filters use op amps (and/or transistors) together with resistors, capacitors, and inductors.

- Allows filters to be designed without inductors
- Op amp characteristics enable design by cascading several “stages”

**Heavy, Bulky,
Expensive**

- **Large Input Impedance**
- **Small Output Impedance**


“First-Order” Lowpass Filter: RC Circuit

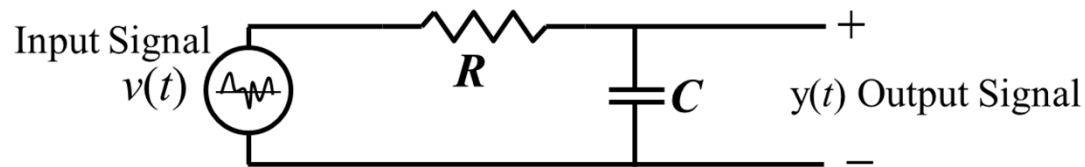

We already analyzed this filter using phasor ideas... but we'll take another look here.

To analyze this filter in the s-domain:

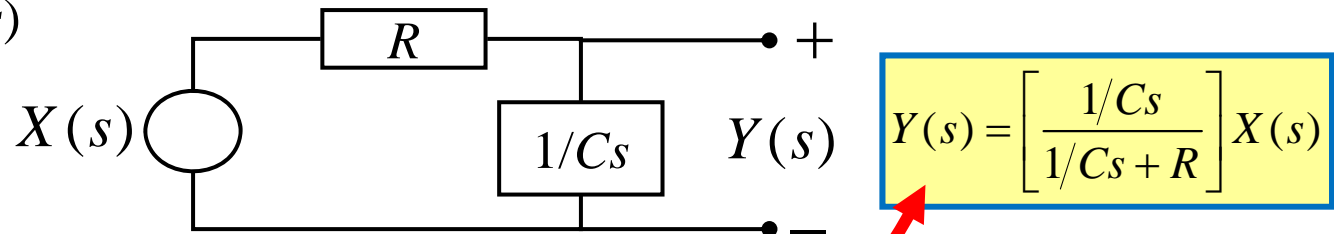- Replace input and output by their LT symbols
- Replace components by their **s-domain impedances**
- Solve for output $Y(s)$ in terms of input $X(s)$... the thing that multiplies $X(s)$ is the TF $H(s)$




By voltage divider (the best approach here) we get this

$$H(s) = \frac{1/Cs}{1/Cs + R}$$

1 Pole @ $s = -1/RC$

$$H(s) = \frac{1}{1 + RCs} = \frac{1/RC}{s + 1/RC}$$

1st Order

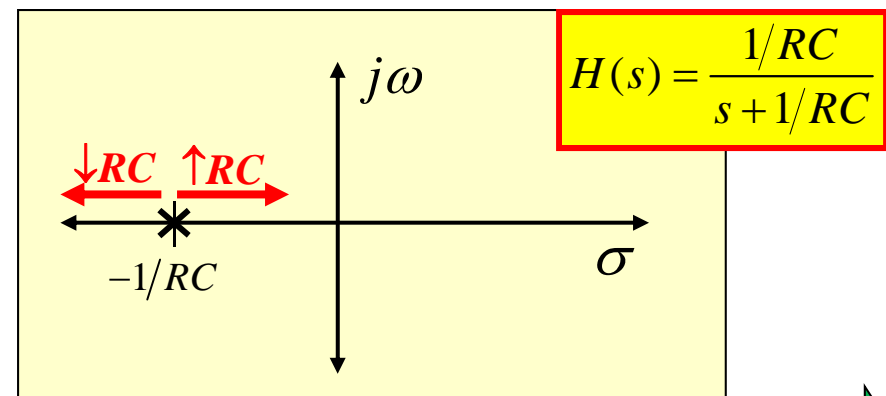

$$H(s) = \frac{1}{1+RCs} = \frac{1/RC}{s+1/RC}$$


$$H(\omega) = \frac{1}{1+jRC\omega}$$

When $\omega = 1/RC$ then
Magn is $1/\sqrt{2}$ (-3dB)




$$|H(\omega)| = \frac{1}{\sqrt{1+(RC)^2 \omega^2}}$$

So... $\omega_c = 1/RC$



$$H(s) = \frac{\omega_c}{s + \omega_c}$$

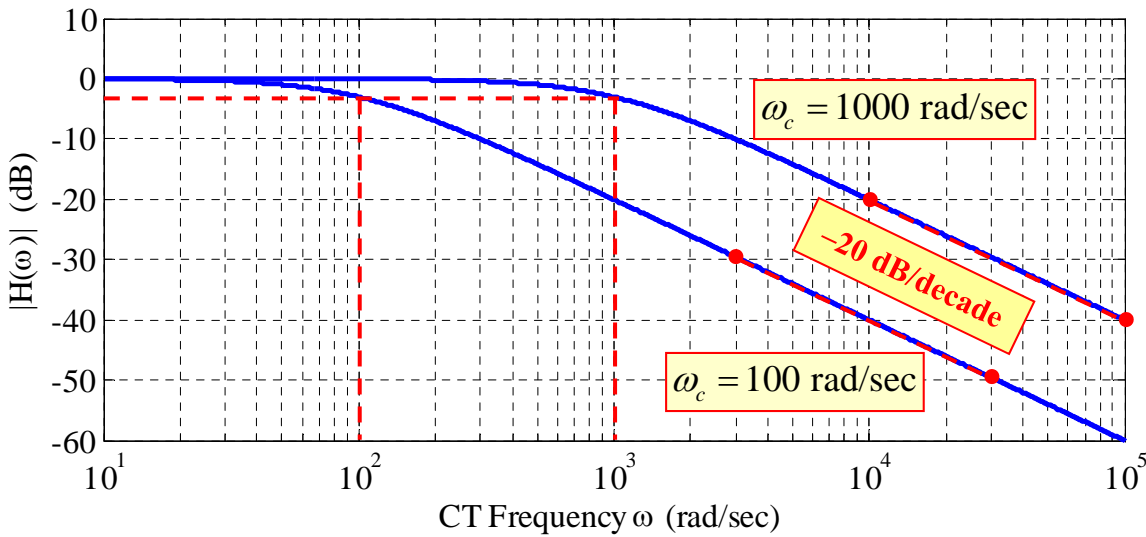
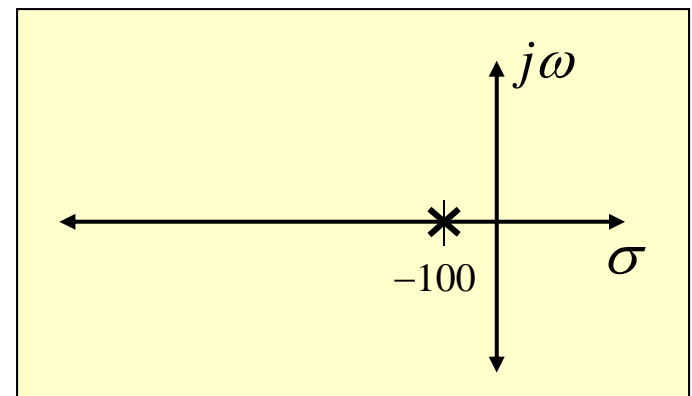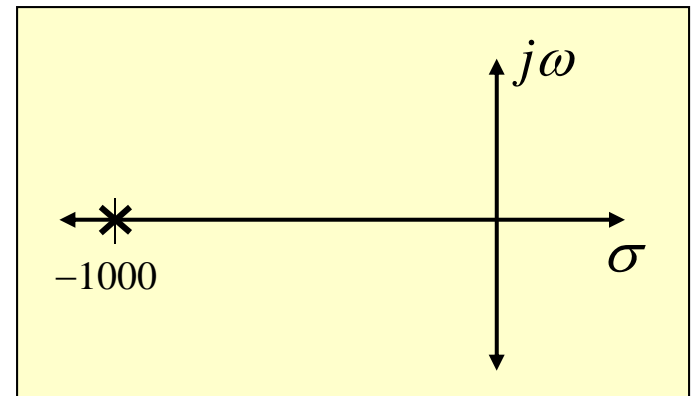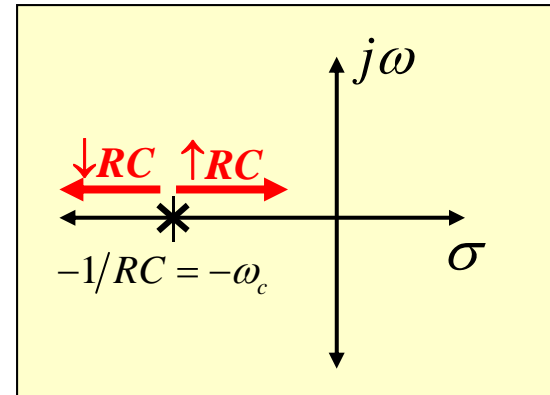
```
>> w=logspace(1,5,1000);
>> wc=100;H=freqs(wc,[1 wc],w);
>> semilogx(w,20*log10(abs(H)))
```



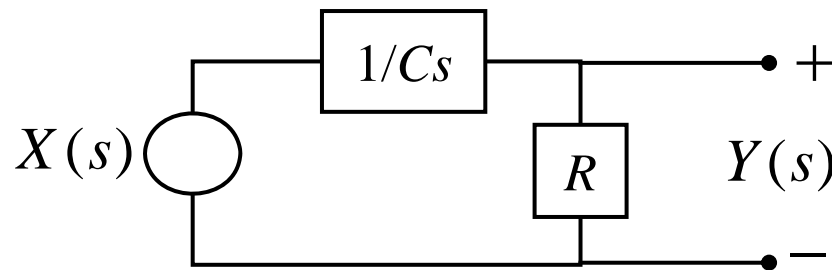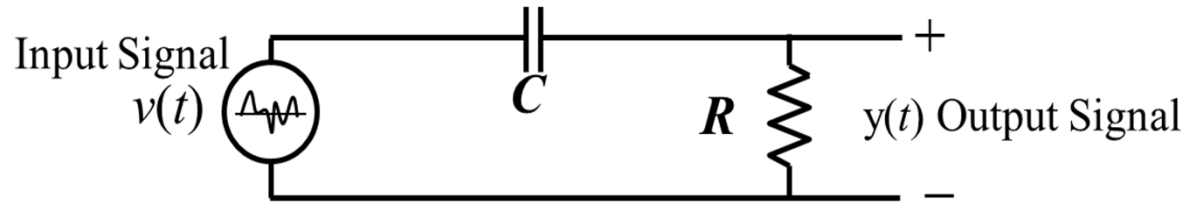“First-Order” Highpass Filter: RC Circuit



$$Y(s) = \left[\frac{R}{1/Cs + R} \right] X(s)$$

By voltage divider (the best approach here) we get this

$$H(s) = \frac{R}{1/Cs + R}$$


↓

$$H(s) = \frac{RCs}{1 + RCs} = \frac{s}{s + 1/RC}$$

1 Zero @ $s = 0$

1st Order

1 Pole @ $s = -1/RC$

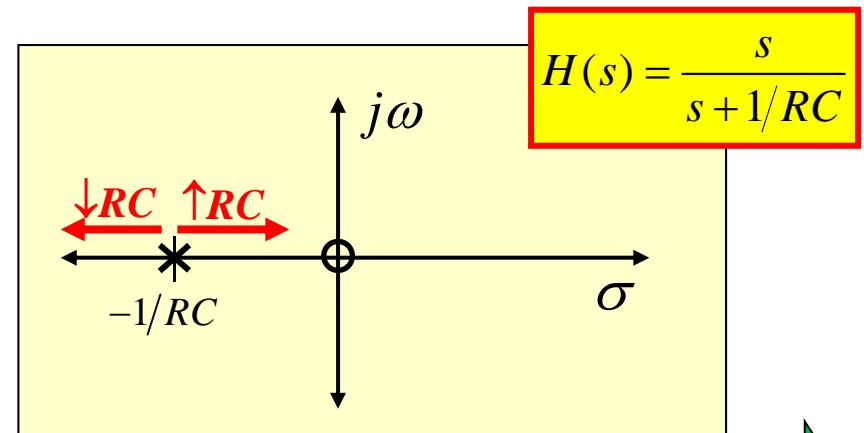

$$H(s) = \frac{RCs}{1 + RCs} = \frac{s}{s + 1/RC}$$


$$H(\omega) = \frac{jRC\omega}{1 + jRC\omega}$$

When $\omega = 1/RC$ then
Magn is $1/\sqrt{2}$ (-3dB)




$$|H(\omega)| = \frac{RC|\omega|}{\sqrt{1 + (RC)^2 \omega^2}}$$

So... $\omega_c = 1/RC$


$$H(s) = \frac{s}{s + \omega_c}$$

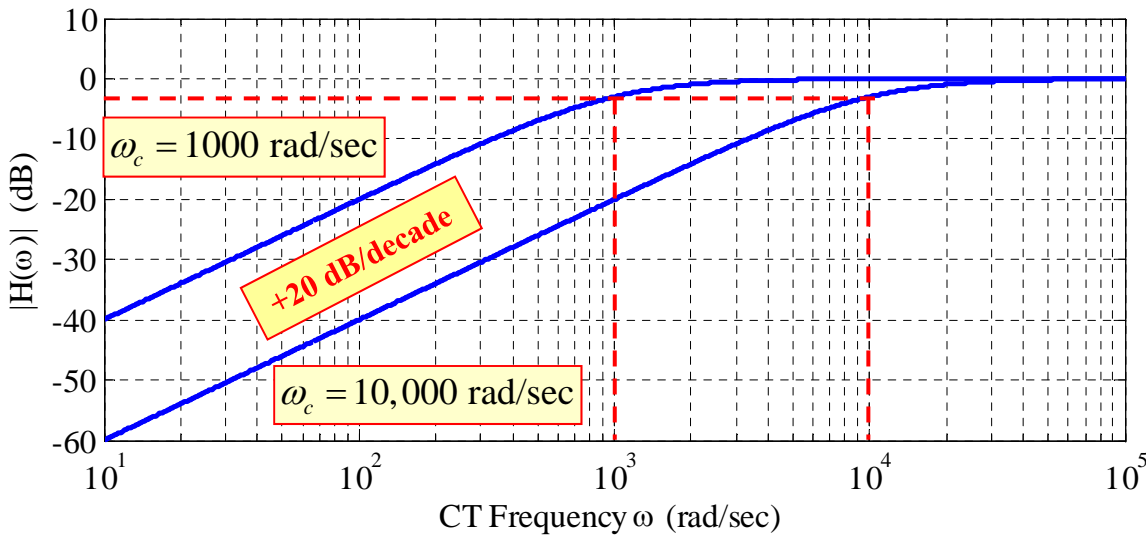
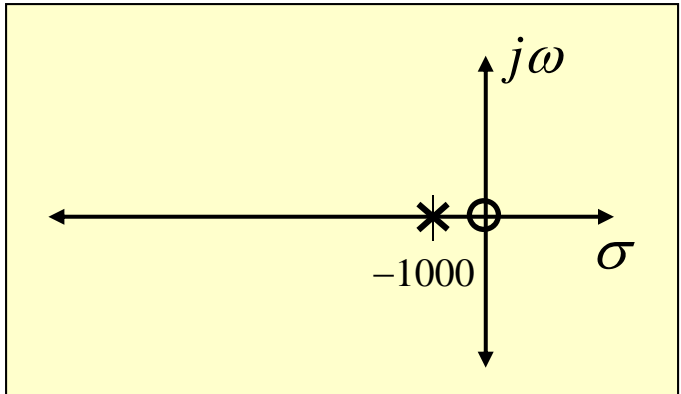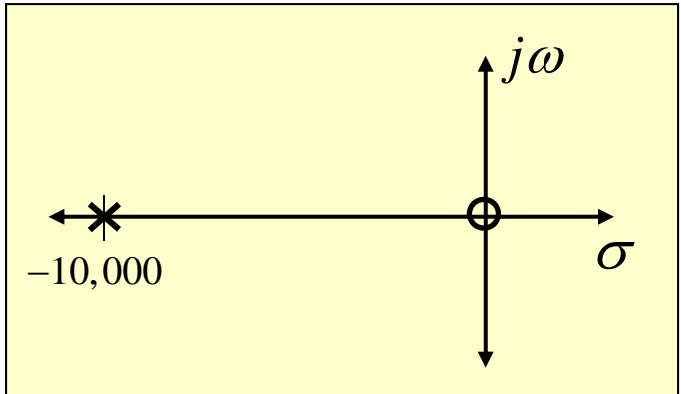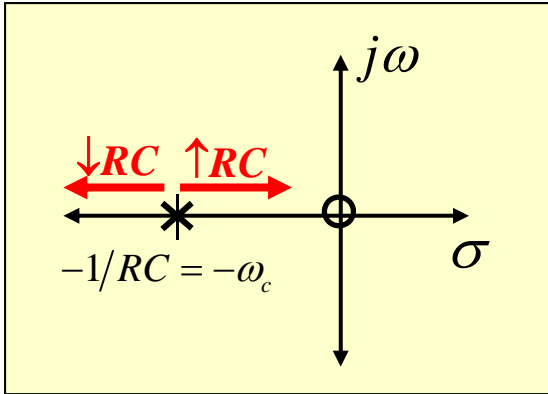
```
>> w=logspace(1,5,1000);
>> wc=1000;H=freqs([1 0],[1 wc],w);
>> semilogx(w,20*log10(abs(H)))
```





Lowpass Filter

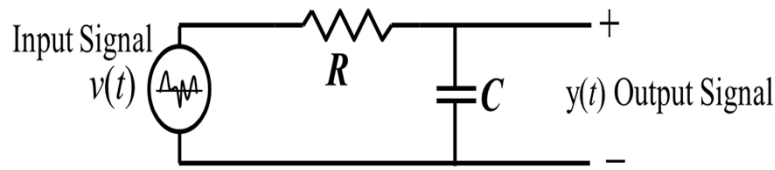


At high freqs... C is like a short...
Stops high frequencies!!

$$H(s) = \frac{\omega_c}{s + \omega_c}$$

$$H(\omega) = \frac{1}{1 + jRC\omega}$$

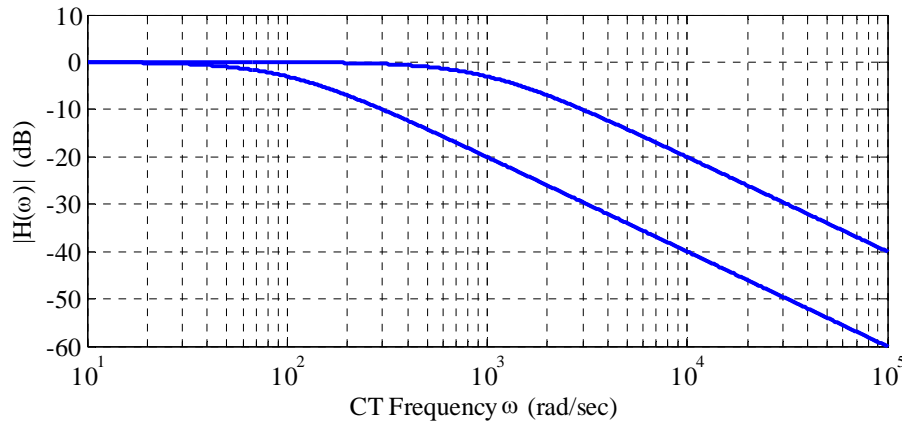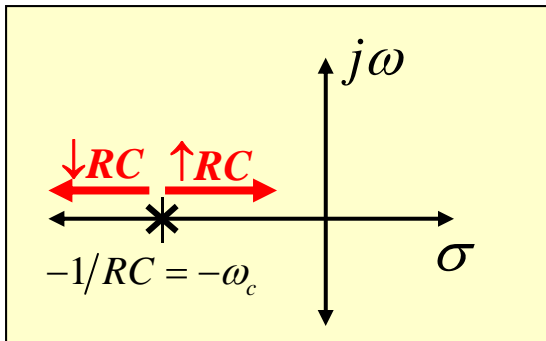



Highpass Filter

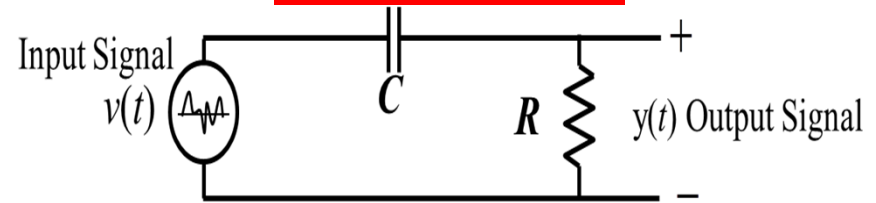



At low freqs... C is like an open...
Stops low frequencies!!

$$H(s) = \frac{s}{s + \omega_c}$$
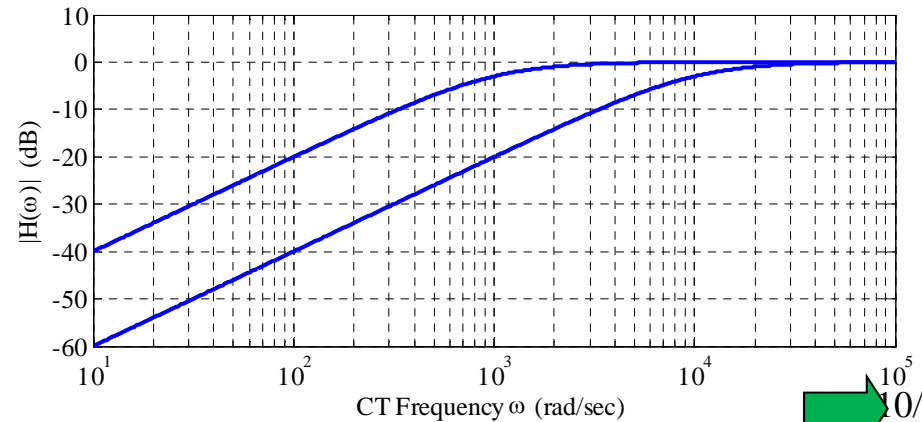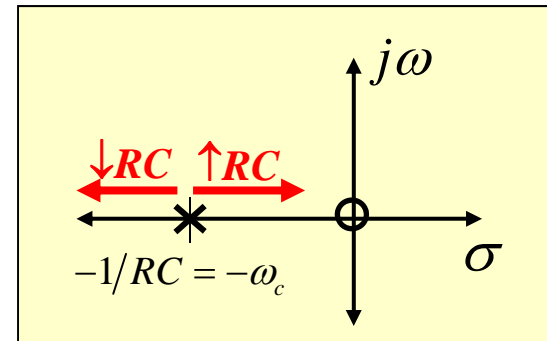
$$H(\omega) = \frac{jRC\omega}{1 + jRC\omega}$$



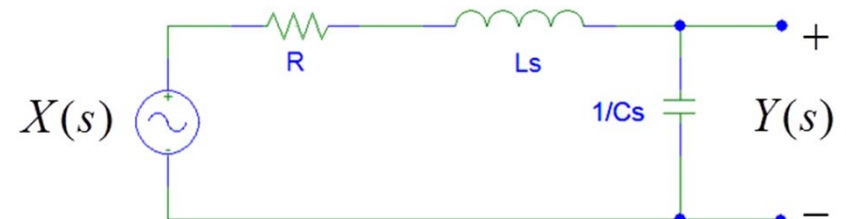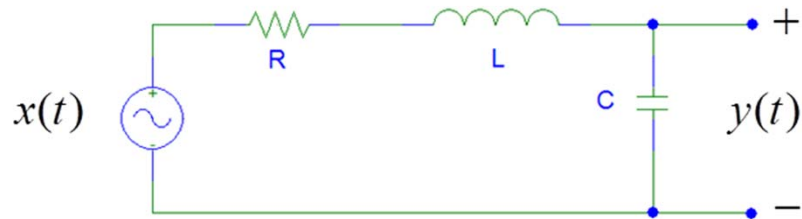
A “Second-Order” **Low**pass Filter: RLC Circuit




By voltage divider (the best approach here) we get this:

$$Y(s) = \left[\frac{1/Cs}{1/Cs + Ls + R} \right] X(s)$$

$$H(s) = \frac{1/Cs}{1/Cs + Ls + R}$$

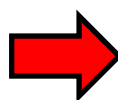
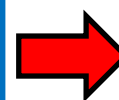
$$H(s) = \frac{1/LC}{s^2 + (R/L)s + 1/LC}$$



$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

2nd Order


**2 Poles
(3 Possible Ways)**

Damping Ratio Natural Freq.


$$\zeta \triangleq \frac{R}{2L}$$

$$\omega_n \triangleq \frac{1}{\sqrt{LC}}$$


Complex-Conjugate Poles

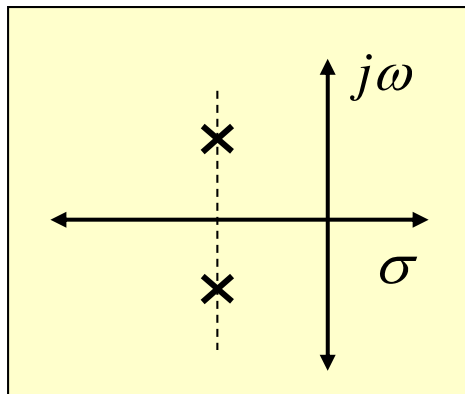

Repeated “Real” Poles

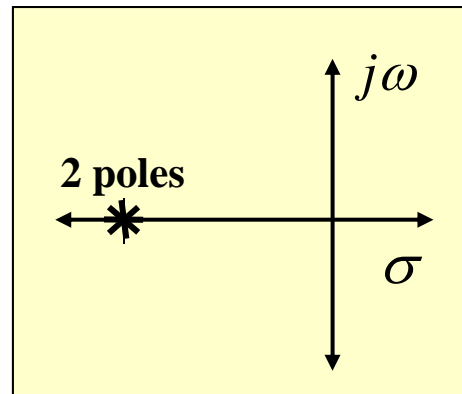

Distinct “Real” Poles

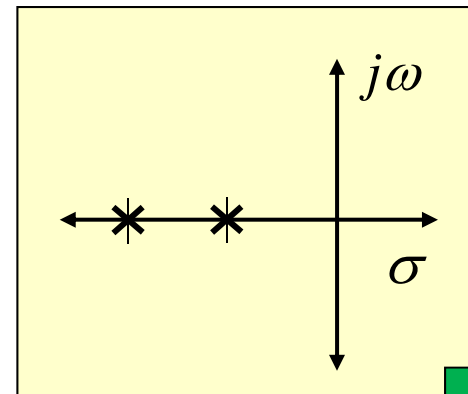


The poles are the roots of $s^2 + (R/L)s + 1/LC$:


$$p_{1,2} = -R/2L \pm \sqrt{(R/2L)^2 - 1/LC}$$

Complex Roots
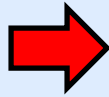
$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$$



$$0 \leq R < \frac{2L}{\sqrt{LC}}$$

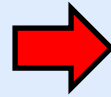


$$0 \leq \zeta < 1$$

$$p_{1,2} = \frac{-R}{2L} \pm j\omega_0$$


$$\omega_0 \triangleq \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

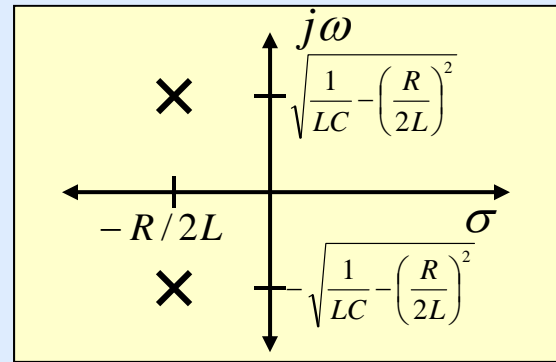When $R = 0$, poles are on $j\omega$ axis




Repeated Real Roots
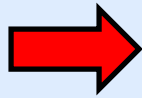
$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$




$$R = \frac{2L}{\sqrt{LC}}$$

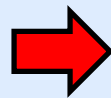


$$\zeta = 1$$

$$p_{1,2} = \frac{-R}{2L}$$

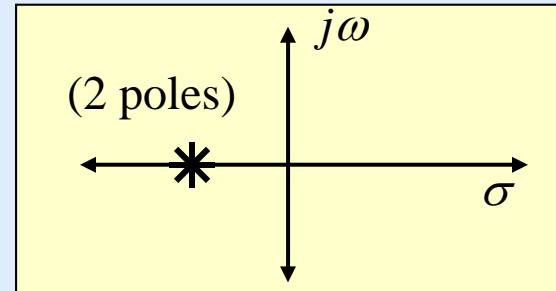

Distinct Real Roots

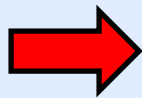
$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$




$$R > \frac{2L}{\sqrt{LC}}$$



$$\zeta > 1$$


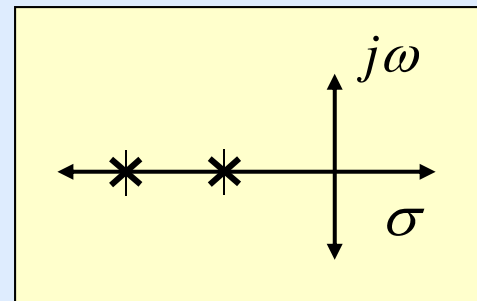


Pole Positions as R is Varied

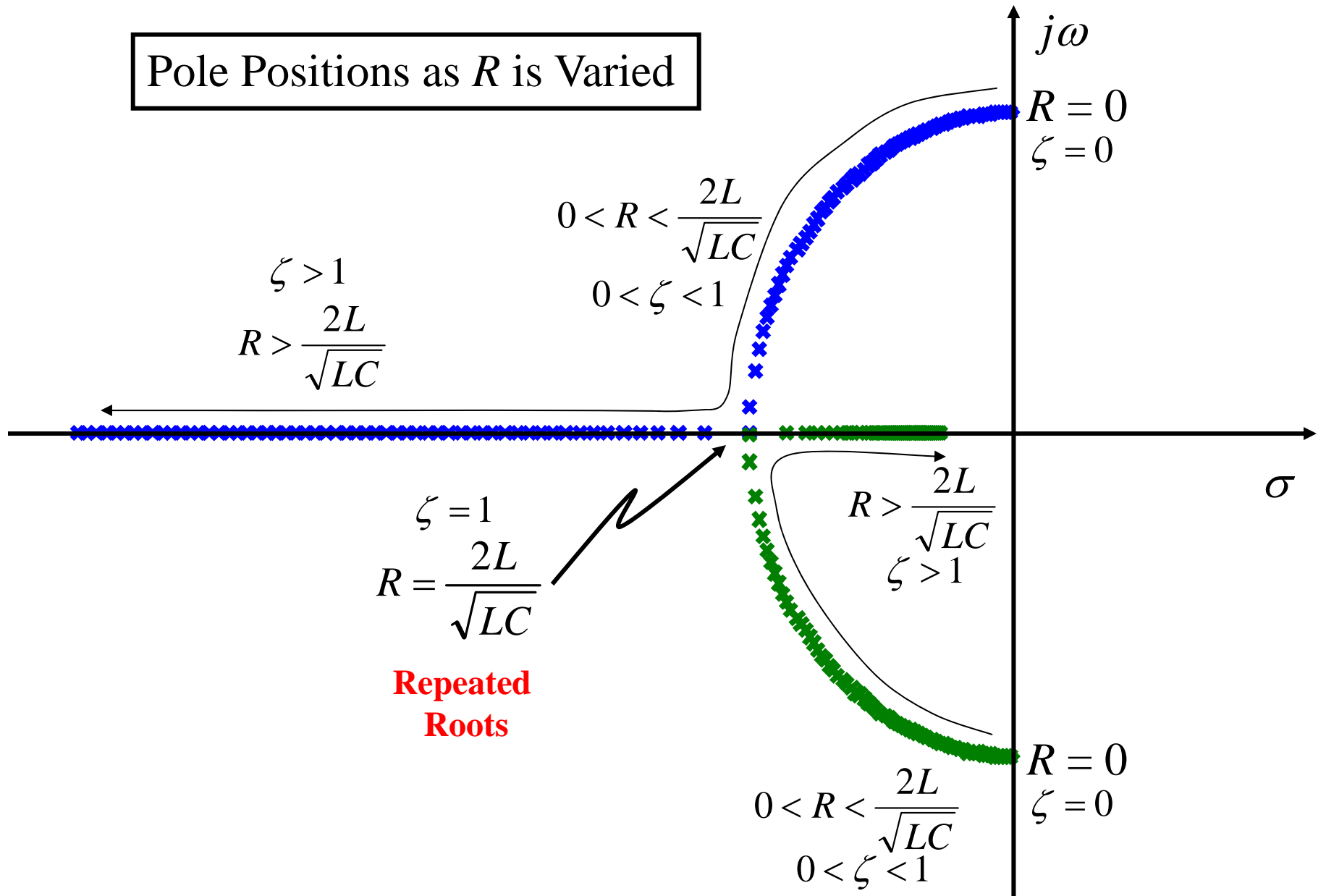

Freq Resp Magnitude for Three Cases
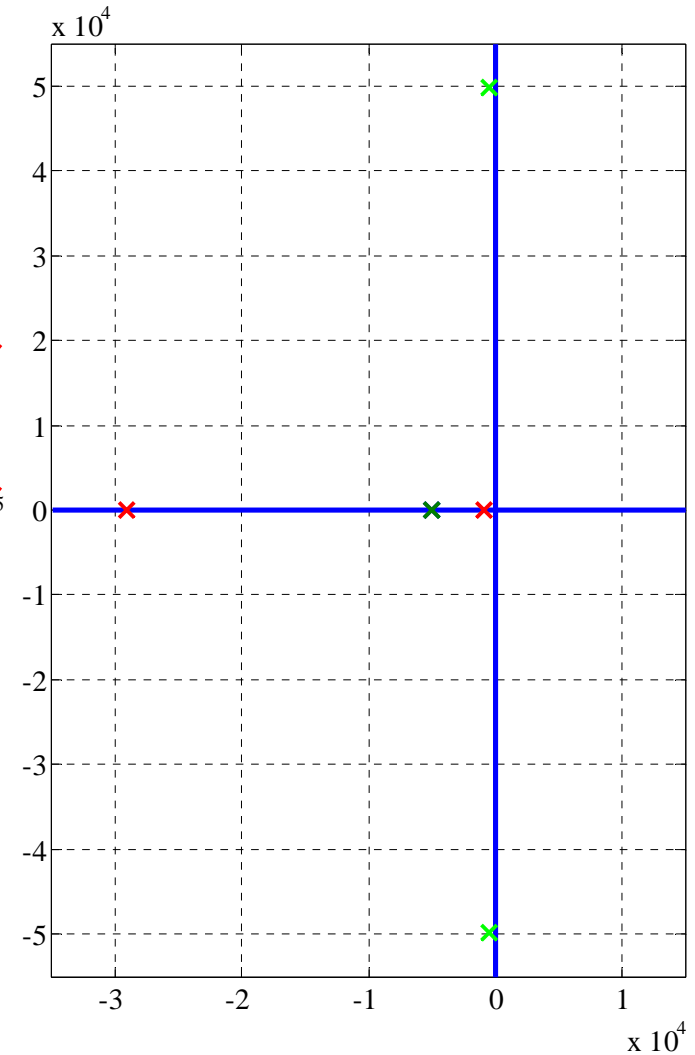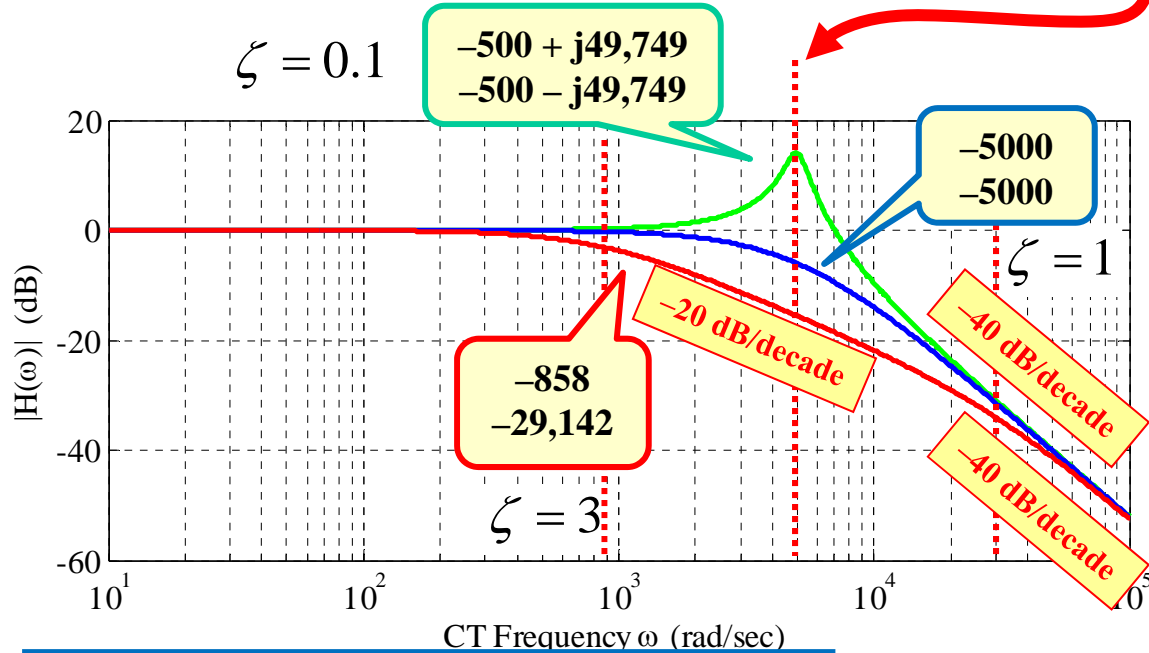
$$\omega_n = \frac{1}{\sqrt{LC}} = 5000 \text{ rad/sec}$$



Complex Poles ($\xi < 1$)

- Peak @ ω_n
- -40 dB/decade slope

Repeated Real Poles ($\xi = 1$)


- “Break” @ ω_n
- -40 dB/decade slope

Distinct Real Poles ($\xi > 1$)

- Two Breaks @ “Poles”
- -20 dB/dec then -40 dB/dec

2nd Order has faster rolloff vs 1st Order
(-40 dB/dec vs. -20 dB/dec)

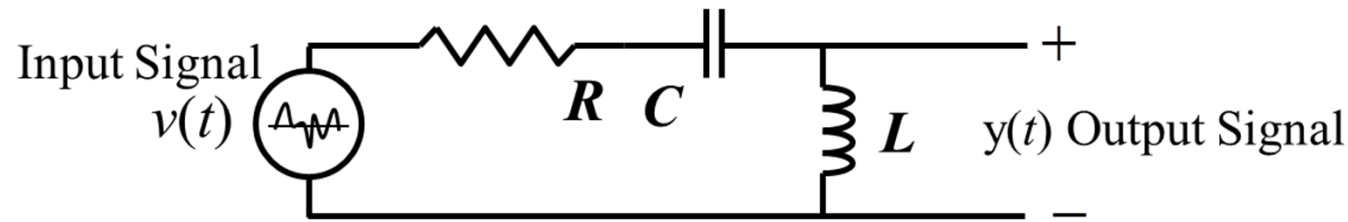A “Second-Order” **High**pass Filter: RLC Circuit



By voltage divider (the best approach here) we get this:

$$Y(s) = \left[\frac{Ls}{1/Cs + Ls + R} \right] X(s)$$

$$H(s) = \frac{Ls}{1/Cs + Ls + R}$$

$$H(s) = \frac{s^2}{s^2 + (R/L)s + 1/LC}$$

$$H(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

2 Zeros @ Origin

Same Denominator!!

2nd Order


2 Poles (3 Possible Ways)

Damping Ratio Natural Freq.


$$\zeta \triangleq \frac{R}{2L}$$

$$\omega_n \triangleq \frac{1}{\sqrt{LC}}$$


Complex-Conjugate Poles

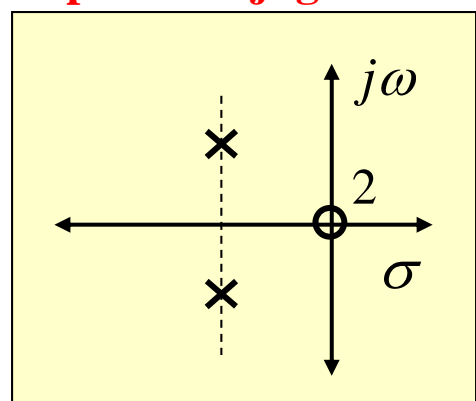


Repeated “Real” Poles

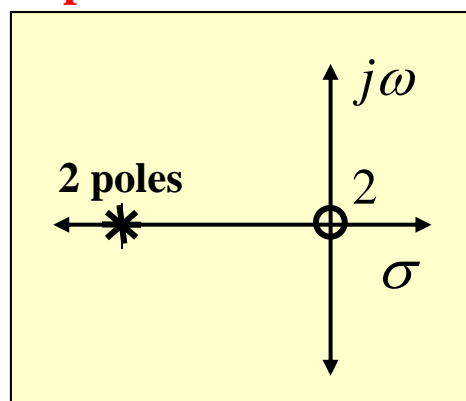

Distinct “Real” Poles

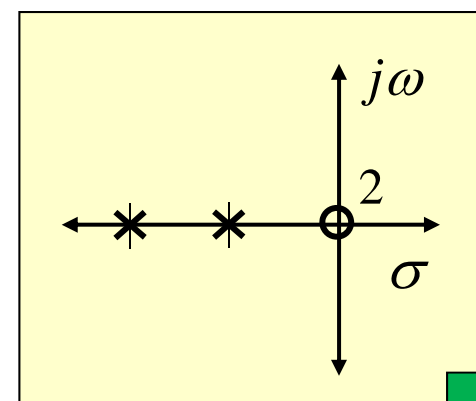

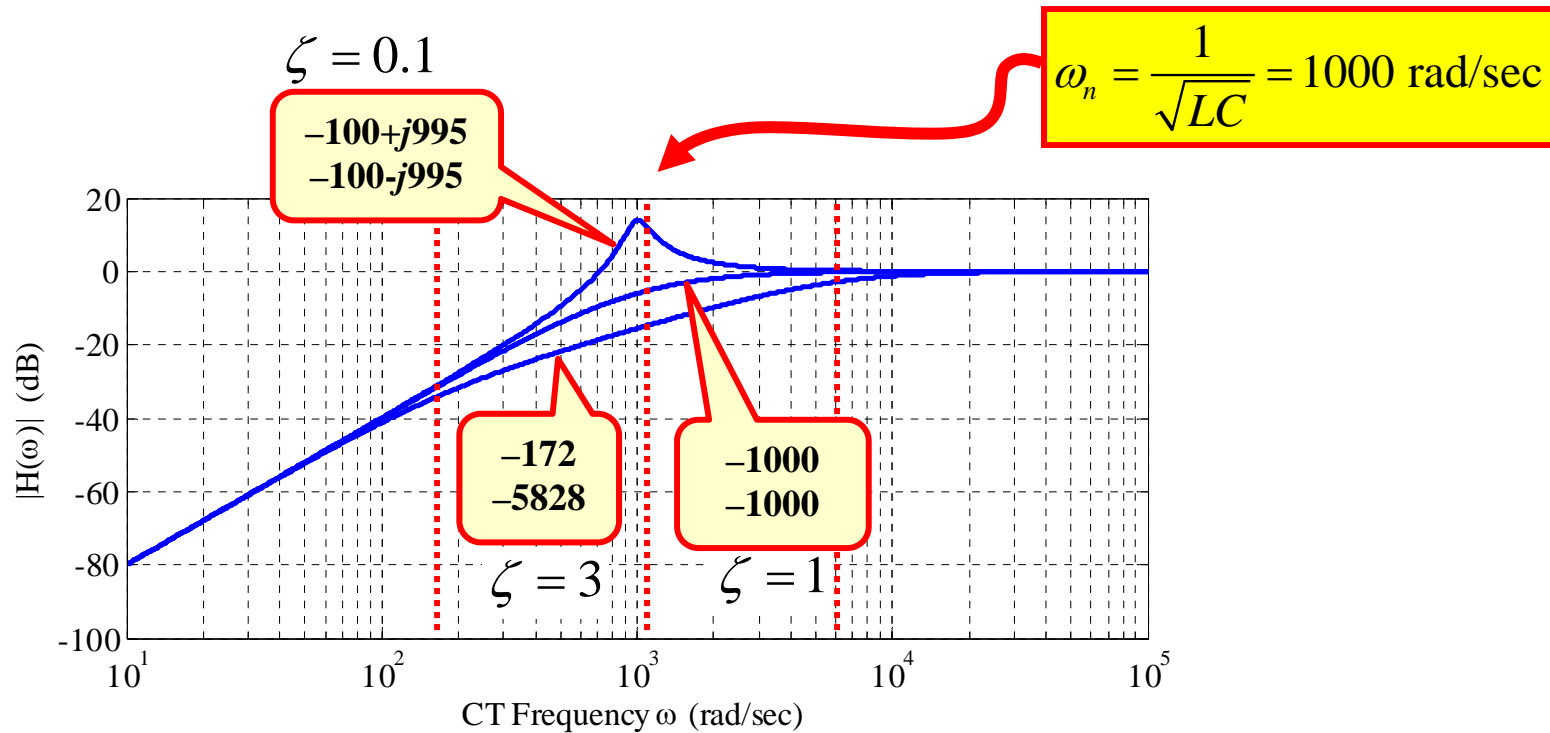


**2nd Order has faster rolloff vs 1st Order
(-40 dB/dec vs. -20 dB/dec)**

**What we are seeing is that we get 20 dB of slope for each order!!!
(For LPF and HPF... But see next for BPF...)**

So a 3rd Order LPF would (eventually) rolloff at -60 dB/decade!!!

So... the main advantage of higher order filters is that your stop band is better due to the faster rolloff!!

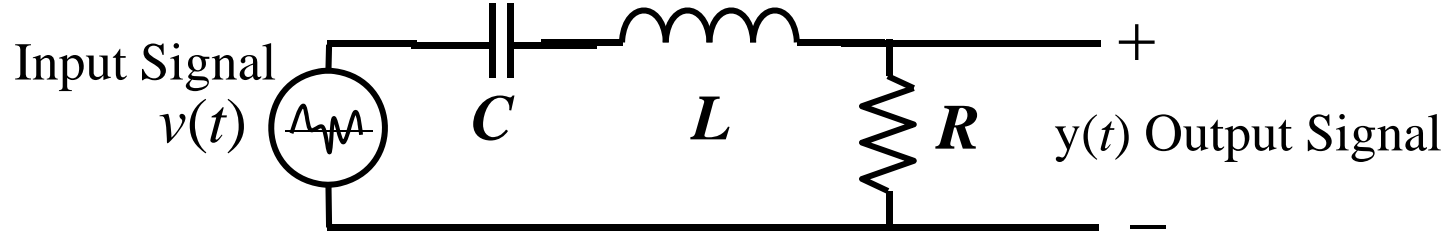A "Second-Order" **Band**pass Filter: RLC Circuit



By voltage divider (the best approach here) we get this:

$$Y(s) = \left[\frac{R}{1/Cs + Ls + R} \right] X(s)$$

$$H(s) = \frac{R}{1/Cs + Ls + R}$$

$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + 1/LC}$$

$$H(s) = \frac{2\zeta\omega_n s}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

1 Zero @ Origin

Same Denominator!!

2nd Order


2 Poles
(3 Possible Ways)

Damping Ratio Natural Freq.


$$\zeta \triangleq \frac{R}{2L}$$

$$\omega_n \triangleq \frac{1}{\sqrt{LC}}$$


Complex-Conjugate Poles

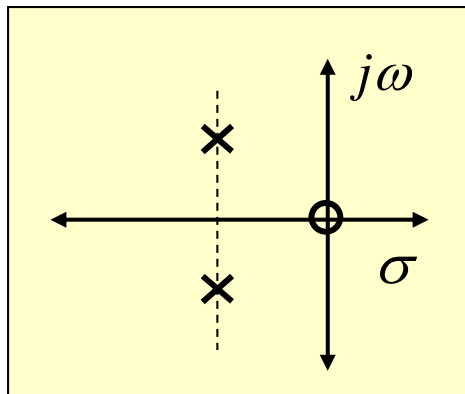


Repeated "Real" Poles

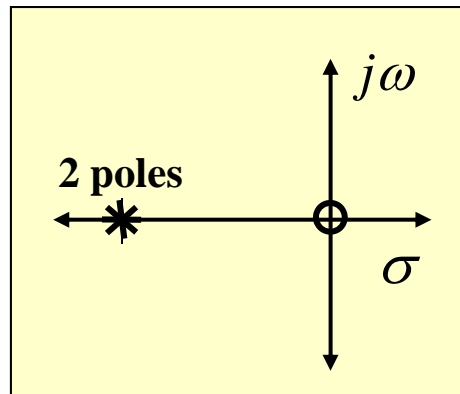

Distinct "Real" Poles

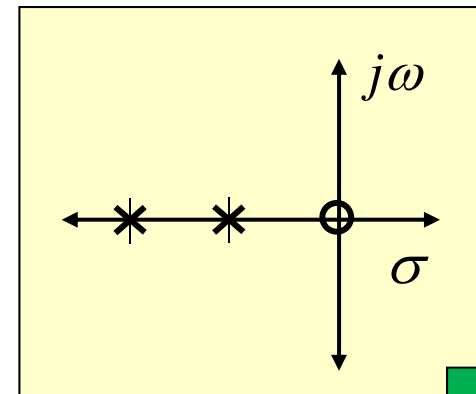

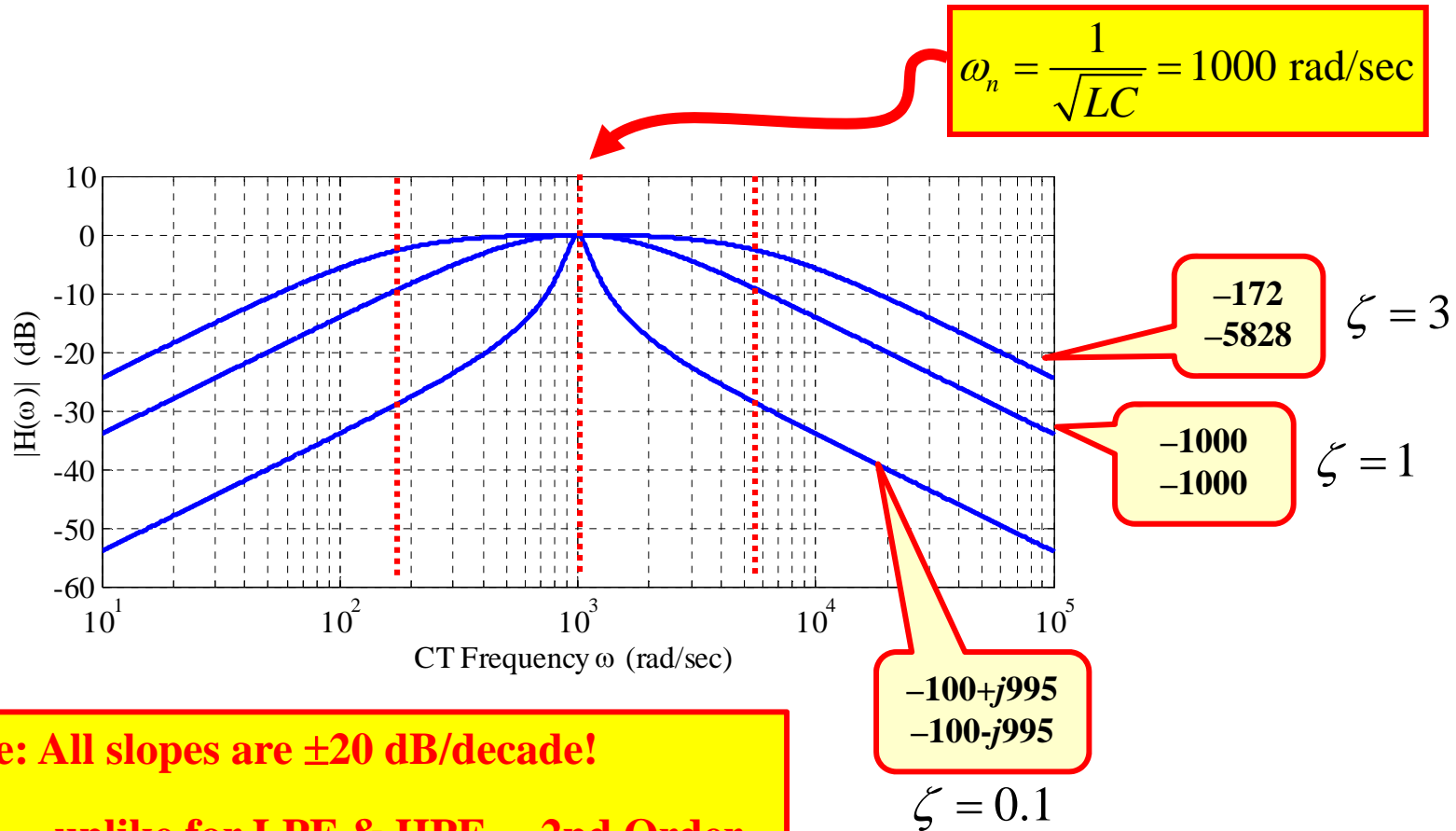

Note: All slopes are ± 20 dB/decade!

So... unlike for LPF & HPF... 2nd Order BPF does NOT have the faster rolloff... But, 1st Order can't even GIVE a BPF!!!

What is happening is that the second order gives you two 20 dB/dec slopes "available"...

But for a BPF you need one going up and one going down... so each only gets one of the two 20 dB slopes!

