

# Examples of Finding Differential Equations for Electrical Systems

For these simple circuits the trick is to first write a KVL or a KCL for the circuit.


Once you have this written identify the parts of it (i.e. voltage and current variables) that **aren't** the input and output signals. You need to find a way to replace these with the input and output signals...

You do this by using:

- "device rules" (like ohms law and the I-V rules for caps and inductors)
- other rules (e.g., if you wrote a KVL first, try writing a KCL and vice versa).

Then simplify it to put it in the standard form

Example: Determine the Diff. Eq.

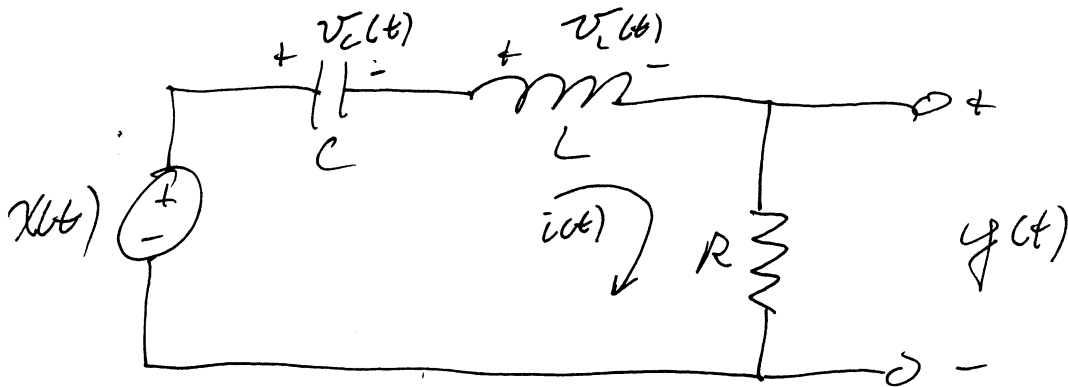

Write KVL around loop:

$$x(t) = v_C(t) + v_L(t) + y(t)$$

$x(t)$  is the input so leave it  
 $y(t)$  is the output so leave it (I screwed up and changed it but I fixed that later)  
 Now...  $V_C$  and  $V_L$  are NOT input or output variables so we need to re-write them in terms of the input and/or output!!  
 a good first step is to use their "device rules" that relate  $V-I$

Should have left this as  $y(t)$ !!!

$$= \frac{1}{C} \int_{-\infty}^t i(\alpha) d\alpha + L \frac{di(t)}{dt} + R i(t)$$

get rid of this by differentiating both sides

Should have this as  $dy(t)/dt$ !!!

$$\Rightarrow \frac{dx(t)}{dt} = \frac{1}{C} i(t) + L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt}$$

Then we notice that we have an integral and we can't have those in a DiffEq so we differentiate get rid of it!!!

These are \*not\* input or output variables so we need to replace them... here there is a simple connection between  $i(t)$  and  $y(t)$


Now relate to output variable:  $y(t) = i(t) R$   
 $\Rightarrow$  replace  $i(t)$  by  $y(t)/R$

$$\Rightarrow \left[ \frac{L}{R} \frac{d^2 y(t)}{dt^2} + \frac{dy(t)}{dt} + \frac{1}{RC} y(t) = \frac{dx(t)}{dt} \right]$$
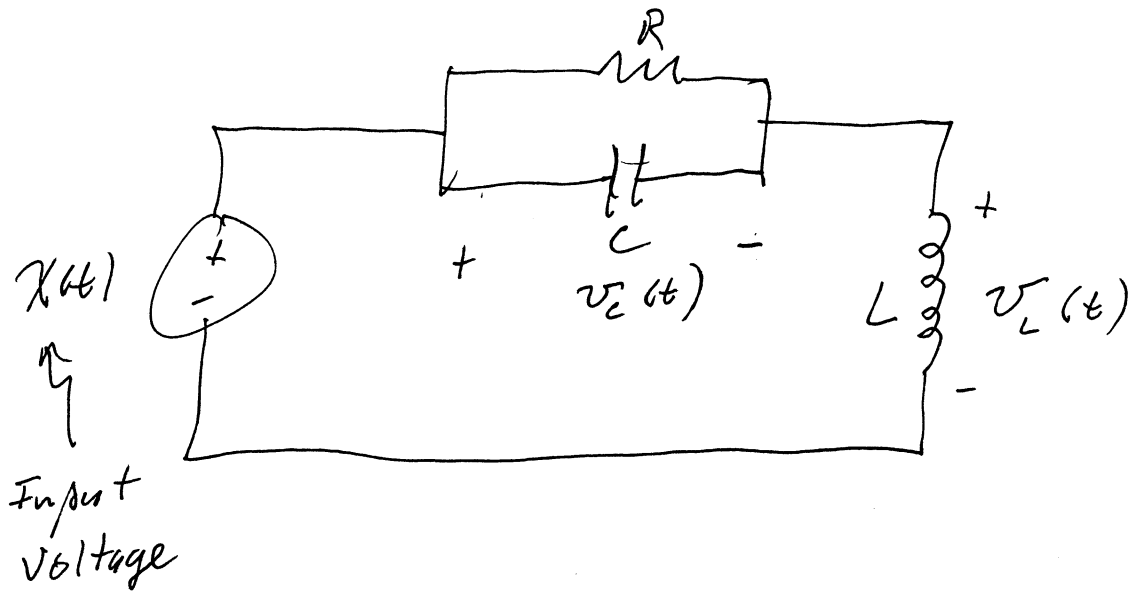
# Example #1

(A)

Determine the differential equation for this circuit ...



(a) ... when  $v_L(t)$  is taken as the output

(b) ... when  $v_C(t)$  is taken as the output

(B)

(a) From KVL:  $v_R(t) + v_L(t) = x(t)$

or  $v_R(t) = x(t) - v_L(t)$   
or  $i_R(t) = \frac{x(t) - v_L(t)}{R}$   
or  $v_L(t) = x(t) - v_R(t)$

From KCL:

Could really start here w/ KCL:

$$i_L(t) = i_R(t) + i_C(t)$$

Now we use KVL and device rules to write as much as we can in terms of input & output

$$i_R(t) = \frac{x(t) - v_L(t)}{R}$$

From KVL above

Device Rule

$$i_C(t) = c \frac{dv_C(t)}{dt}$$
  
$$i_C(t) = c \left[ \frac{dx(t)}{dt} - \frac{dv_L(t)}{dt} \right]$$

Now we have something that is almost completely in terms of in's & out's so we are almost there!!!

$$i_L(t) = \frac{x(t) - v_L(t)}{R} + c \frac{dx(t)}{dt} - c \frac{dv_L(t)}{dt} \quad (*)$$

We need one more device rule...

in terms of in's & out's

Must relate to in's/out's

Device Rule

$$\frac{di_L(t)}{dt} = \frac{1}{L} v_L(t)$$

We do this differentiation so we can plug this device rule in!!! When we do that we get the equation below

$$\frac{1}{L} v_L(t) = \frac{1}{R} \frac{dx(t)}{dt} - \frac{1}{R} \frac{dv_L(t)}{dt} + c \frac{d^2x(t)}{dt^2} - c \frac{d^2v_L(t)}{dt^2}$$

so diff. right side of (\*)

(C)

Re arrange to get:

$$\frac{d^2 v_L(t)}{dt^2} + \frac{1}{RC} \frac{dv_L(t)}{dt} + \frac{1}{LC} v_L(t) = \frac{d^2 x(t)}{dt^2} + \frac{1}{RC} \frac{dx(t)}{dt}$$

(b) From KVL:  $v_C(t) + v_L(t) = x(t) \Rightarrow v_L(t) = x(t) - v_C(t)$

From device Rule for L:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

use KCL:  $i_L(t) = i_R(t) + i_C(t)$

$$= L \left[ \frac{di_R(t)}{dt} + \frac{di_C(t)}{dt} \right]$$

$$\Rightarrow x(t) - v_C(t) = L \frac{di_R(t)}{dt} + L \frac{di_C(t)}{dt}$$

$$i_R(t) = \frac{v_R(t)}{R}$$

$$= \frac{v_C(t)}{R}$$

$$i_C(t) = C \frac{dv_C(t)}{dt}$$



$$x(t) - v_C(t) = \frac{L}{R} \frac{dv_C(t)}{dt} + LC \frac{d^2 v_C(t)}{dt^2}$$


Re-Arrange:

$$\frac{d^2 v_C(t)}{dt^2} + \frac{1}{RC} \frac{dv_C(t)}{dt} + \frac{1}{LC} v_C(t) = \frac{1}{LC} x(t)$$
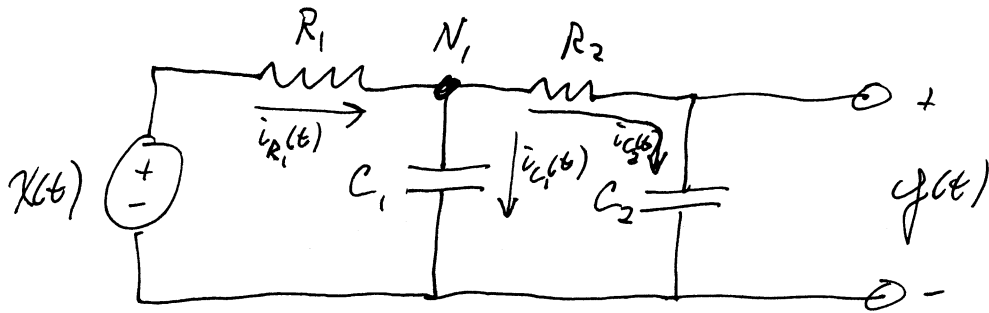
## Example #2

(D)

Write the Diff. Eq. for the following "2-stage" RC circuit:



Node Eq. at  $N_1$ : (Node Equations are a form of KCL)

$$\begin{aligned} \underbrace{\dot{i}_{R_1}(t)} &= \underbrace{\dot{i}_{C_1}(t)} + \underbrace{\dot{i}_{C_2}(t)} \\ \downarrow & \qquad \qquad \downarrow \\ \frac{x(t) - v_{C_1}(t)}{R_1} &= C_1 \frac{dv_{C_1}(t)}{dt} + C_2 \frac{dy(t)}{dt} \end{aligned} \quad (\star)$$

Almost have what we want... need to get  $v_{C_1}(t)$  out of the equation!

KVL around 2nd Mesh

$$\begin{aligned} v_{C_1}(t) &= v_{R_2}(t) + y(t) \\ &= R_2 \dot{i}_{C_2}(t) = R_2 \left[ C_2 \frac{dy(t)}{dt} \right] \end{aligned}$$

(\*\*)  
Use all this to eliminate  $v_{C_1}(t)$

Put ~~(A)~~ into (A) to get:

(E)

First re-write (A):

$$C_2 \frac{dy(t)}{dt} + C_1 \frac{dv_{c_1}(t)}{dt} + \frac{1}{R_1} v_{c_1}(t) = \frac{1}{R_1} x(t)$$

From ~~(A)~~ we get:

$$v_{c_1}(t) = R_2 C_2 \frac{dy(t)}{dt} + y(t)$$

and

$$\frac{dv_{c_1}(t)}{dt} = R_2 C_2 \frac{d^2 y(t)}{dt^2} + \frac{dy(t)}{dt}$$


We get:

$$C_1 R_2 C_2 \frac{d^2 y(t)}{dt^2} + \left( C_1 + \frac{R_2 C_2}{R_1} + C_2 \right) \frac{dy(t)}{dt} + \frac{1}{R_1} y(t) = \frac{1}{R_1} x(t)$$

which could then be normalized by multiplying by  $1/C_1 R_2 C_2$

# DC Motor Example ("Armature Control")

(F)

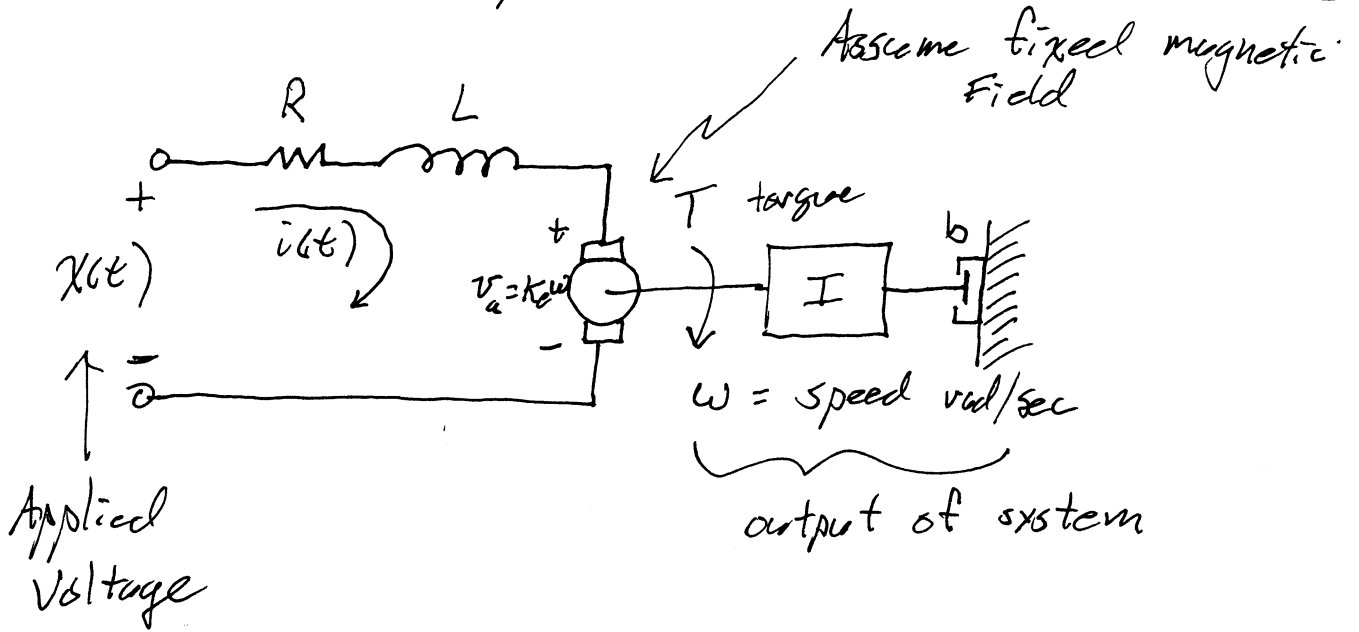

- DC Motor consists of lots of wire wound on an "armature"  $\Rightarrow$  motor has "parasitic"  $R \ \& \ L$
- As motor armature turns, the coils cut magnetic flux lines  $\Rightarrow$  induces voltage proportional to speed  

$$v_a(t) = k_e \omega(t)$$

Now write KVL around the armature circuit:

$$x(t) = R i(t) + L \frac{di(t)}{dt} + k_e \omega(t) \quad (*)$$

- The current  $i(t)$  in the windings interacts w/ the magnetic field to create a force which provides the motor torque  $T(t)$

$$T(t) = k_t i(t) \quad (**)$$



Finally, rotational mechanics provides

(6)

$$T(t) = I \frac{d\omega(t)}{dt} + b\omega(t) \quad (\text{A A A})$$

$\underbrace{\hspace{10em}}$   
Torque due to Mass I      Torque due to friction

Putting (A A A) into (A A) and dividing by  $K_t$  gives:

$$i(t) = \frac{I}{K_t} \frac{d\omega(t)}{dt} + \frac{b}{K_t} \omega(t)$$

Now put this in (A) to get:

$$\frac{LI}{K_t} \frac{d^2\omega(t)}{dt^2} + \left(\frac{RI + LIb}{K_t}\right) \frac{d\omega(t)}{dt} + \left(K_t + \frac{Rb}{K_t}\right) \omega(t) = X(t)$$

$\Rightarrow$  Second-Order Diff. Eq.

$\Rightarrow$  Could be Oscillatory!

